

8-bit Counter Project

Perform the following tasks:

1. Write Verilog code describing an 8-bit programmable binary counter with asynchronous reset, synchronous load and tri-state outputs.
2. Show that the Verilog code works (test it!).
3. Build using github actions in Tiny Tapeout for the GF-180nm technology.
4. Due date on github: September 24.